


LAB#2

(Due Date & Time: See course web page)

Instructor: Dr. Choon Kim

Objective

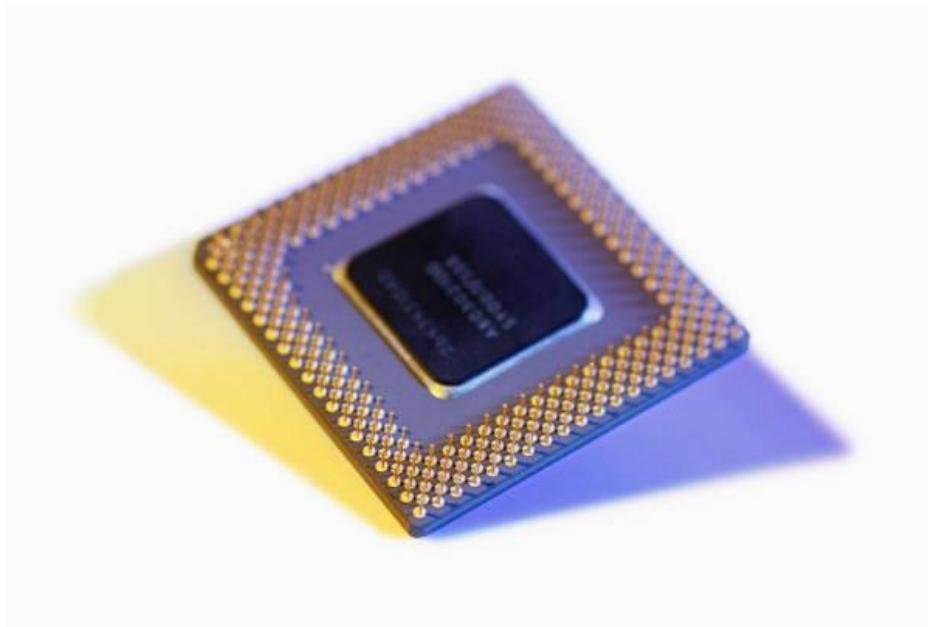- Based on the experience gained from LAB#1, learn how to design, simulate, synthesize, program on FPGA and test **combinational & sequential** digital components using Altera Quartus II CAD SW and DE1 FPGA board.
- Learn and become familiar with digital logic design using **Verilog Hardware Description Language**



Instructions

1. Your LAB#2 project name should be **L2Cyyy**, where yyy=your CID(e.g., **L2C079** if your CID=079). The golden solution [.pof](#) and [.sof](#) files are provided.

Student should play with golden solution as a reference whenever he/she has a question during design.


2. Use Verilog HDL design. Use the following Verilog top-level module interface code for your design. **No part of this code is allowed to be modified.** The top-level module name must be same as your LAB project name.

```
module L2Cyyy(           // where yyy=your CID. e.g., L2C079 if your CID=079
    input  [9:0] sw,      // ten up-down switches, SW9 - SW0
    input  [3:0] key,     // four pushbutton switches, KEY3 - KEY0
    input   clock,        // 24MHz clock source on Altera DE1 board
    output [9:0] ledr,    // ten Red LEDs, LEDR9 - LEDR0
    output [7:0] ledg,    // eight Green LEDs, LEDG8 - LEDG0
    output reg [6:0] hex3, hex2, hex1, hex0    // four 7-segment, HEX3 - HEX0
);
```

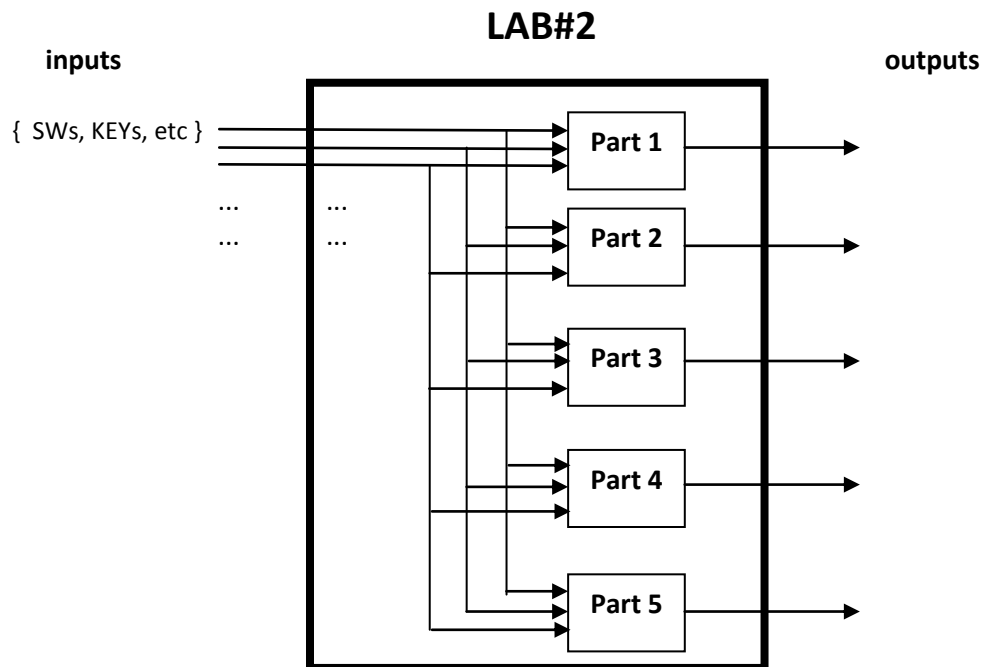3. Our acceptable timing margin for real-time clock operation is -30 and +30%.

For example, for 1-second period required in Part4&5 of this LAB, a time period between 0.7 sec(= -30%) and 1.3 sec(= +30%) is acceptable as a 1-second period. A time period beyond this range is unacceptable as 1-second period.

Similar to LAB#1, LAB#2 has a following structure (See each Part for details).



4. LAB#2 Project Operations(**These operations are prerequisite conditions for all Parts**)

When power is turned on, your DE1 board must be in the following **initial state**:

- all SWs are in DOWN position
- all keys are NOT PRESSED
- all leds(ledg and ledr) are OFF
- No Part of this LAB is enabled
- hex[3]=OFF(no light), hex[2:0] displays your CID. For example, HEX[3:0]= **097** if your CID=097. The *Golden solution* displays HEX[3:0]= **353** since it's CID=353.

The **sw[9:5]** is a Part selector. You enable or disable a particular Part by setting the sw[9:5] as follows. No more than one switch on sw[9:5] is allowed to be in UP position(i.e., no more than one Part is enabled at the same time!).

```
IF sw[9:5]=00000 // all sw are in DOWN position
    Initial state AND all Parts are disabled

ELSE IF sw[9:5]=00001 // only sw[5] is in UP position
    Part1 is enabled AND all other Parts are disabled

ELSE IF sw[9:5]=00010 // only sw[6] is in UP position
    Part2 is enabled AND all other Parts are disabled

ELSE IF sw[9:5]=00100 // only sw[7] is in UP position
    Part3 is enabled AND all other Parts are disabled

ELSE IF sw[9:5]=01000 // only sw[8] is in UP position
    Part4 is enabled AND all other Parts are disabled

ELSE IF sw[9:5]=10000 // only sw[9] is in UP position
    Part5 is enabled AND all other Parts are disabled
```

Warning: Above operations are prerequisite conditions. You will get **zero(0) point** for LAB#2 if you fail above operations **regardless of Parts**.

PART 1 (Basic) Decimal and Hex Number Display design

Design a **Decimal** and **Hex** Number Display circuit as follows.

Inputs: SW[3:0] // four-bit binary number input
Output: HEX[3:0] // displays Decimal and Hex numbers

Operation

If **Part1** is enabled // see Sec. 4. LAB#2 Project Operations

HEX[3:2] => displays a **Decimal** number of SW[3:0].

HEX[1] => OFF(no light).

HEX[0] => displays a **Hex** number of SW[3:0].

***** The End of Part1 *****

Hints

For example,

SW[3:0]	HEX[3:2]	HEX[0]
0000	00	0
0001	01	1
0010	02	2
0011	03	3
.....		
.....		
.....		
1000	08	8
1001	09	9
1010	10	A
1011	11	b // <--- use lower case!
1100	12	C
1101	13	d // <--- use lower case!
1110	14	E
1111	15	F



PART 2 (Basic) Adder/Multiplier design

Design an Adder/Multiplier circuit as follows.

Inputs: SW[4:3] = operand1 in binary
SW[2:1] = operand2 in binary
SW[0] is an operation selector: 0 for **Addition**, 1 for **Multiplication**

Output: HEX[3] = Decimal value of operand1
HEX[2] = Decimal value of operand2
HEX[1] = OFF(i.e., no light)
HEX[0] = Decimal value of Result

Operation:

If **Part2** is enabled // see Sec. 4. LAB#2 Project Operations

HEX[3:0] displays values defined above Adder/Multiplier circuit

***** **The End of Part2** *****

----- *Hints* -----

For example,

SW[4:0]	HEX[3:0]	
00000	00 0	// addition...
00010	01 1	
01010	11 2	
10100	22 4	
11100	32 5	
11110	33 6	
.....		
00001	00 0	// multiplication...
00011	01 0	
01011	11 1	
10101	22 4	
11101	32 6	
11111	33 9	
.....		



PART 3 (Intermediate) Modulo-16 Up/Down Counter design

Design a Modulo-16 Up/Down Counter circuit as follows.

Inputs: KEY[2] for **input**. An input is entered to counter **each time** the key is **pressed down** (Note that **NO** input is entered when the key is **released**).
SW[0] for **reset** operation (0 for normal counting, 1 for **clearing the counter output to zero**)
SW[1] for selecting direction of counting (0 for **Up**, 1 for **Down** counting)
(SW[1] changes the direction of counting **at any moment** during operation.)

Output: HEX[2] = counter output in **hex**.
All other HEXs = OFF(no light),

Operation:

If **Part3** is enabled // see Sec. 4. LAB#2 Project Operations

- 1) The **initial value** of HEX[2] must be **0** when sw[7] goes up(i.e., when Part3 is enabled)
- 2) Your circuit counts the number of pressing on KEY[2] and displays the result on HEX[2]. Therefore HEX[2] **increases** or **decreases** each time KEY[2] is pressed depending on SW[1].
- 3) SW[1] changes the direction of counting **at any moment** during operation.
- 4) Your counter output should work as Modulo-16 operation.
- 5) SW[0] is a **reset** switch. If SW[0]=0, the counter operates normally. If SW[0]=1 then the counter output HEX[2] is cleared to 0 and the counting function is **not** performed.

***** **The End of Part3** *****

----- *Hints* -----

For example,

Case1) When **sw[1]=0**, **0** => 1 => 2 => 3 => ... => d => E => F => **0** => 1 => 2 => 3 =>...

Case2) When **sw[1]=1**, **0** => F => E => d => ... => 3 => 2 => 1 => **0** => F => E => d => ...

Case3) A new counting starts with **sw[1]=0**, HEX[2] starts from 0(by reset), **0** => 1 => 2 => 3 => ... => d => E => F => **0** => 1 => 2 => 3 **here, sw[1]=1** 3 => 2 => 1 => **0** => F => E => d => ... => 3 => 2 => 1 => **0** => F => E => d **here, sw[1]=0** d => E => F => **0** => 1 => 2 => 3 =>.....



PART 4 (Intermediate) Real-Time Measurement Circuit design

Design a Real-Time Measurement Circuit as follows.


Inputs: SW[0] for reset

Output: HEX[3:0] for measurement output (in Modulo-3 operation)
LEDG[0] for blinking signal

Operation

If Part4 is enabled // see Sec. 4. LAB#2 Project Operations

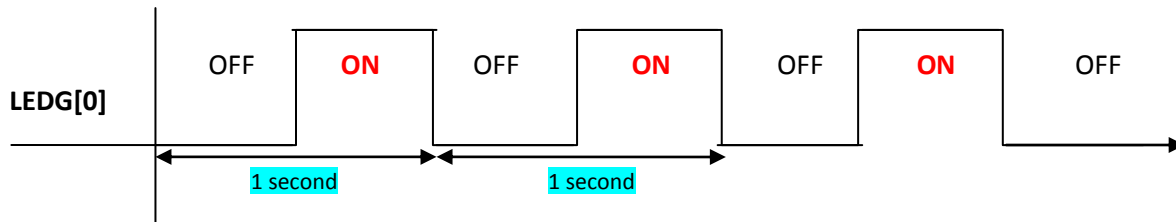1. HEX[3:0] starts displaying the number of seconds passed **since the moment when SW[8] goes up**(i.e., when Part4 enabled). Each HEX digit displays the counter output in Modulo-3 operation.
2. The LEDG[0] starts blinking every second with 50% duty cycle as follows.



3. SW[0] is a reset switch. If SW[0]=0, the timer operates normally. If SW[0]=1 then HEX[3:0] is **cleared to 0000**, LEDG[0]= OFF(no light), and the time measurement function is not performed.

***** The End of Part4 *****

----- Hints -----

- 1) DE1 User manual sec. 4.4. for **clock operation** may be helpful
- 2) For example ,

```
HEX[3:0] = 0000 // <---- when SW[8] goes up here! (i.e., Part4 enabled)
HEX[3:0] = 0001 // after one second passed
HEX[3:0] = 0002 // after another second passed(i.e., two seconds passed)
HEX[3:0] = 0010 // after another second passed(i.e., three seconds passed),
HEX[3:0] = 0011 ....
HEX[3:0] = 0012
HEX[3:0] = 0020
HEX[3:0] = 0021
....
HEX[3:0] = 2222
HEX[3:0] = 0000 // <----back to 0000, Modulo-3 operation!
```

PART 5 (***Advanced & Challenging!***)



Bouncing Ball with Moving Message Display design

Design a Bouncing ball with Moving message circuit as follows.

Inputs: SW[0] for **pausing** the operation(0 for resume operation, 1 for **pausing**)

Output: LEDR[9:0] for bouncing ball
HEX[3:0] for moving message

Operation

If **Part5** is enabled // see Sec. 4. LAB#2 Project Operations

1. [Bouncing Ball on LEDR[9:0]]
Starting from LEDR[0] position, a red light ball moves from LEDR[0] to LEDR[9] with a duration of **0.5 second**. When arrived at LEDR[9], the ball moves from LEDR[9] back to LEDR[0] with same duration of **0.5 second**. Therefore the time period of one round trip is **one(1) second**.
When returned to LEDR[0], the red light ball keeps repeating the same movement.
2. [Moving Message on HEX[3:0]]
A message, " HELLO Cid <yourCID> ", is moving from right to left repeatedly. For example, "**HELLO Cid 353**" in golden solution.
The message movement is synchronized to the bouncing ball. **The message moves one letter whenever the bouncing ball hits the LEDR[9](=left edge).**
3. SW[0] is a **pause** switch(it's not a **reset** switch!).
SW[0] = 1 pauses the operation.
SW[0] = 0 resumes the operation.

***** **The End of Part5** *****

----- *Hints* -----

Knowledge of handling clock operation learned from Part4 may be helpful for this Part also.

----- **The End of LAB#2** -----